
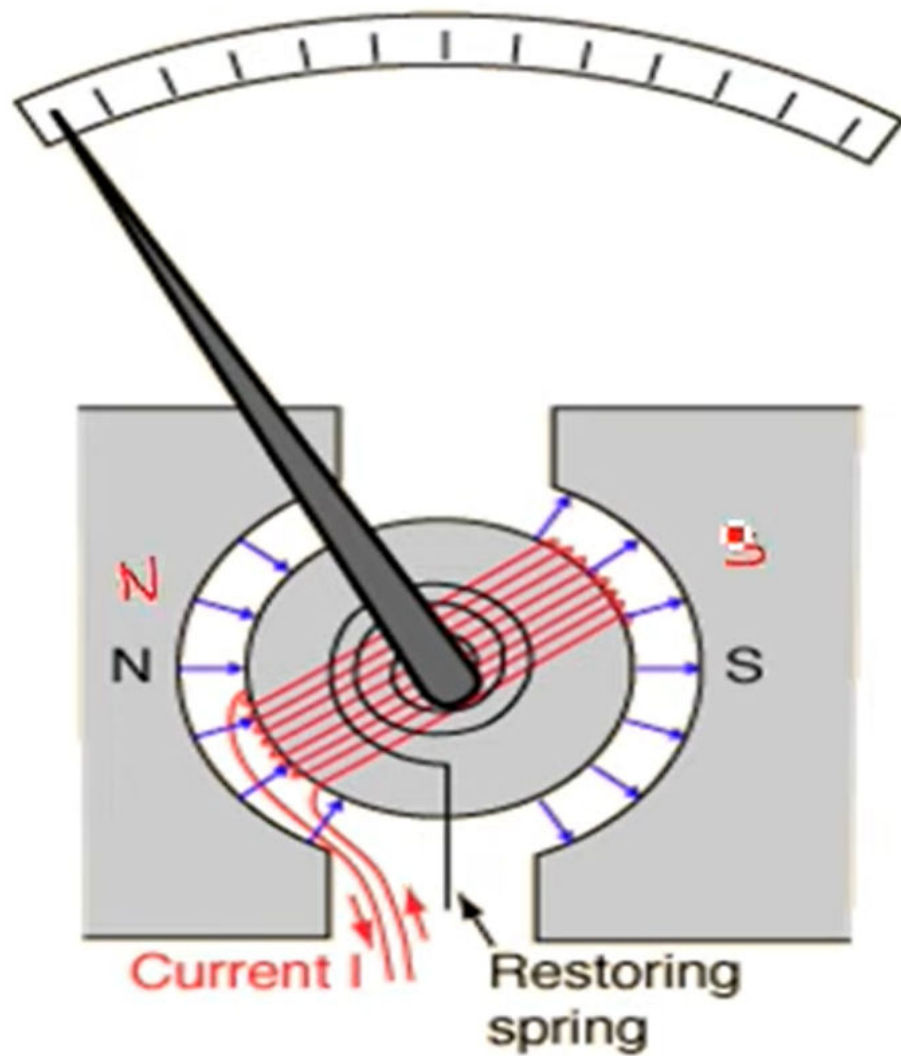


Basic meter

- D'Arsonval
- PMMC
- Galvanometer.

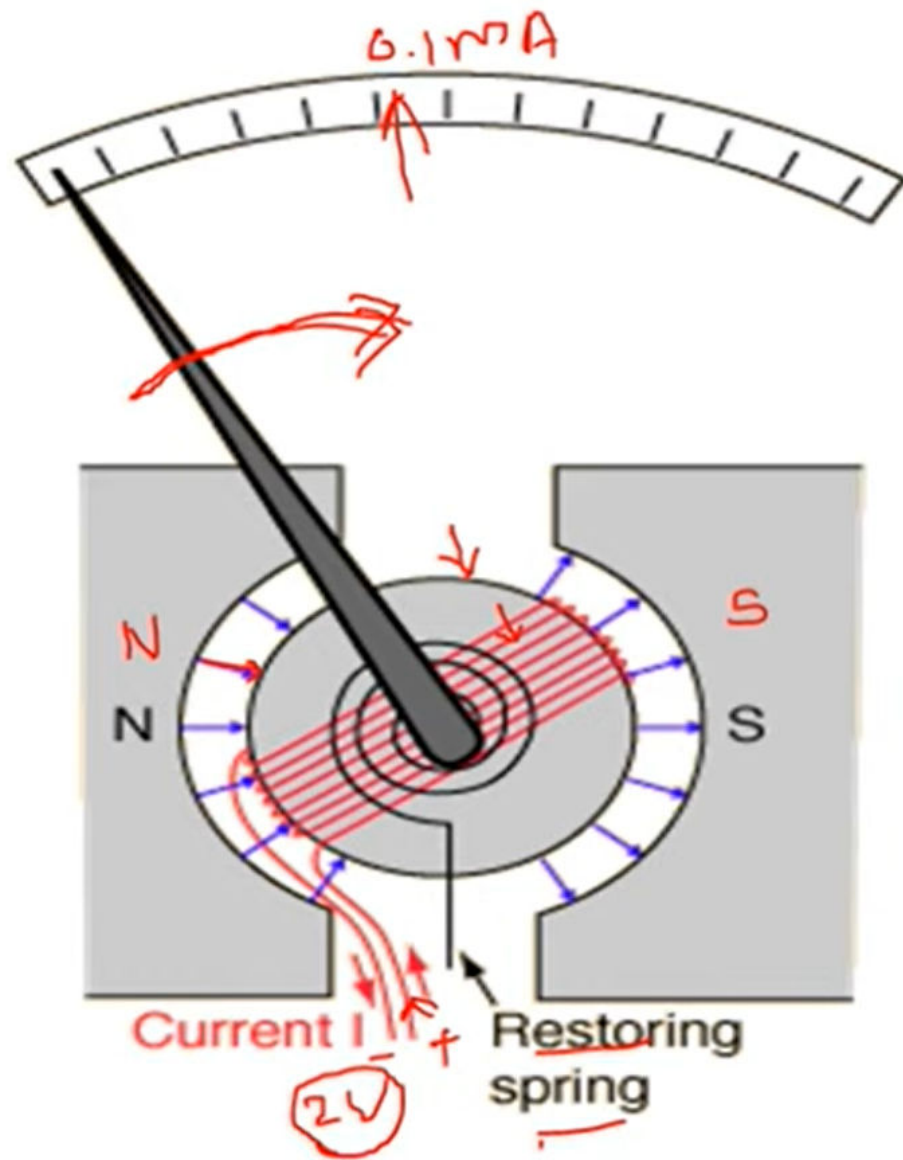

Basic meter



- D'Arsonval
- PMMC
- Galvanometer.

$$\tau \propto A \cdot I \cdot N$$

$$\tau = B \times A \times I \times N$$

$B \rightarrow$ flux density (wb/m^2)


$A \rightarrow$ Area of the coil (m^2)

$I \rightarrow$ Current flowing (A)

$N \rightarrow$ no. of turns

$$\gamma \rightarrow \text{wb} - \text{A}.$$

DC Ammeter

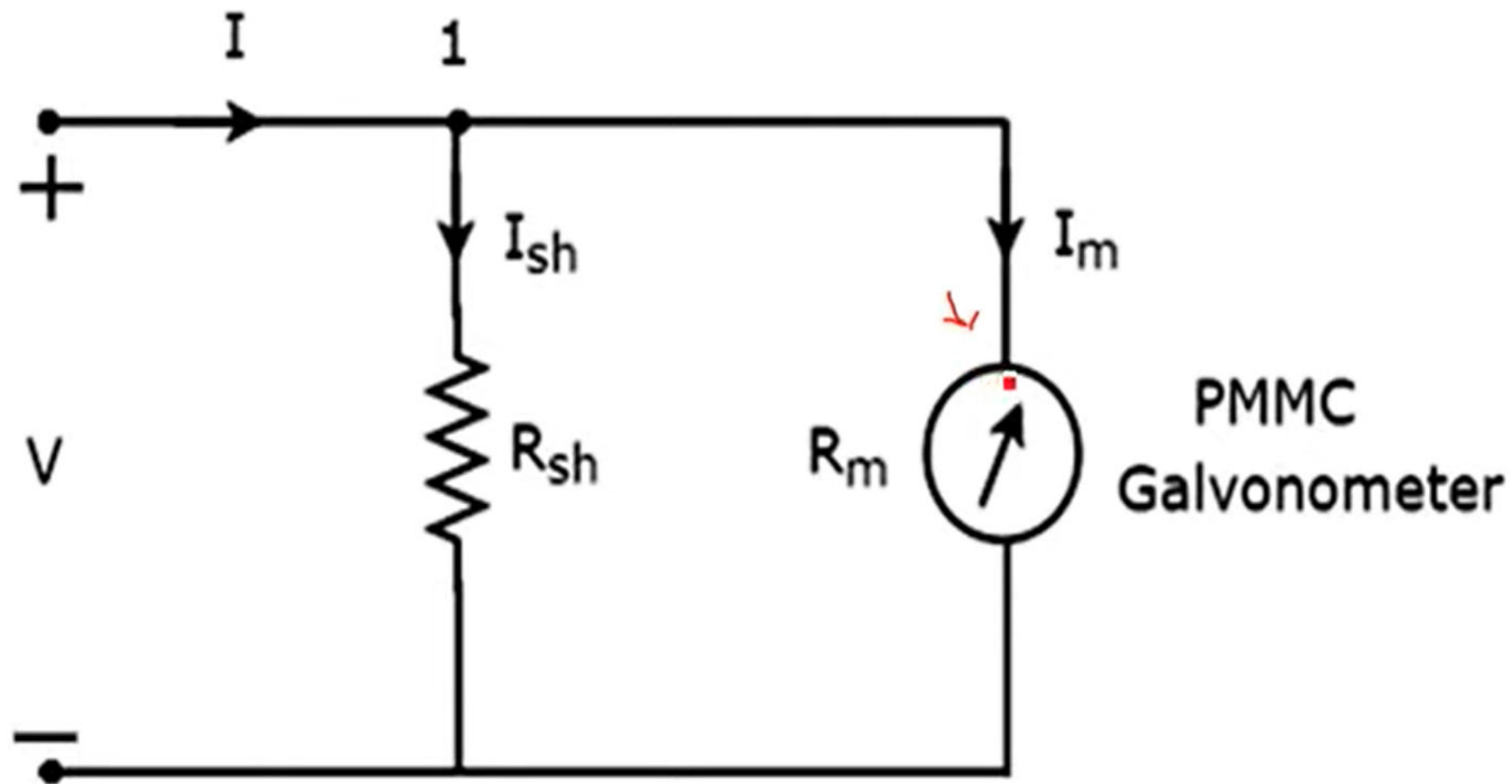

Referring to Fig.:

R_m = internal resistance of the movement

R_{sh} = shunt resistance

I_{sh} = shunt current

I_m = full scale deflection current of the movement


I = full scale current of the ammeter + shunt (i.e. total current)

voltage is same in parallel.

$$I_{sh} R_{sh} = I_m R_m$$

$$I_{sh} = I - I_m$$

$$R_{sh} = \frac{I_m R_m}{I - I_m}$$

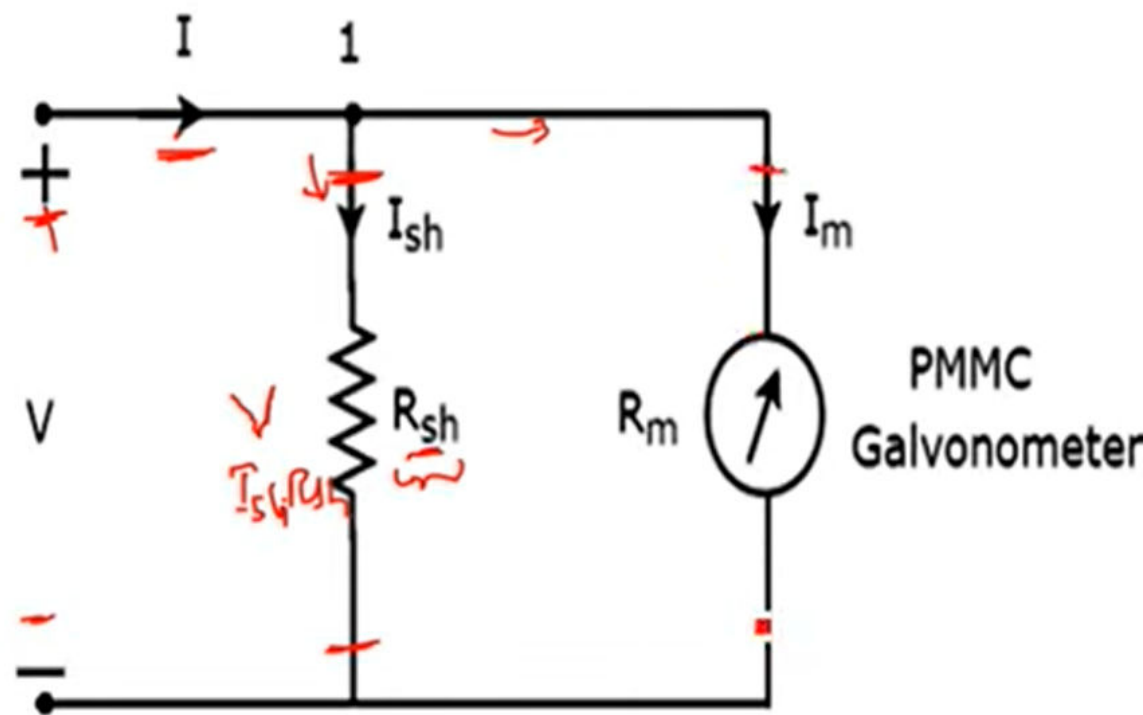

Example Problem

1. A 1mA meter movement with an internal resistance of 100Ω is to be converted into a 0-100 mA. Calculate the value of shunt resistance required.

Example Problem


1. A 1mA meter movement with an internal resistance of 100Ω is to be converted into a 0-100 mA. Calculate the value of shunt resistance required.

$$I_m = 1\text{mA}, \quad R_m = 100\Omega, \quad I = 100\text{mA}.$$

$$R_{sh} = \frac{I_m \cdot R_m}{I - I_m} = \frac{1 \times 10^{-3} \times 100}{100\text{mA} - 1\text{mA}} = \frac{0.1}{99\text{mA}} = 1.01\Omega$$

$$\boxed{R_{sh} = 1.01\Omega}$$

DC multi-range ammeter

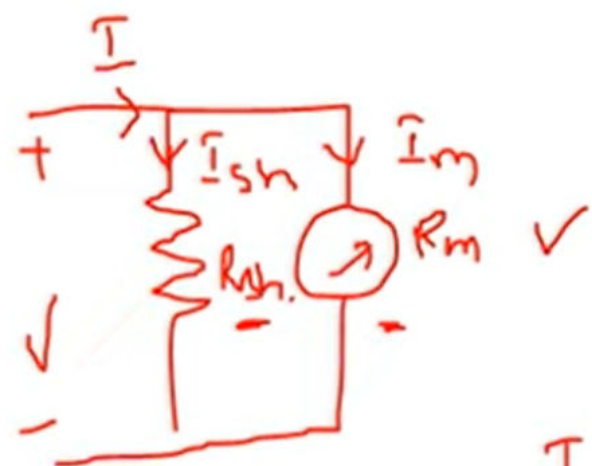

→ single.
↳ R_{sh} .


$$I = I_{sh} + I_m$$

$R_{sh} \downarrow \uparrow \rightarrow I_{sh} \uparrow \downarrow$

DC multi-range ammeter

- The range of the dc ammeter is extended by a number of shunts, selected by a range switch.
- The resistors is placed in parallel to give different current ranges.
- Switch S (multi-position switch) protects the meter movement from being damage during range changing.

DC multi-range ammeter

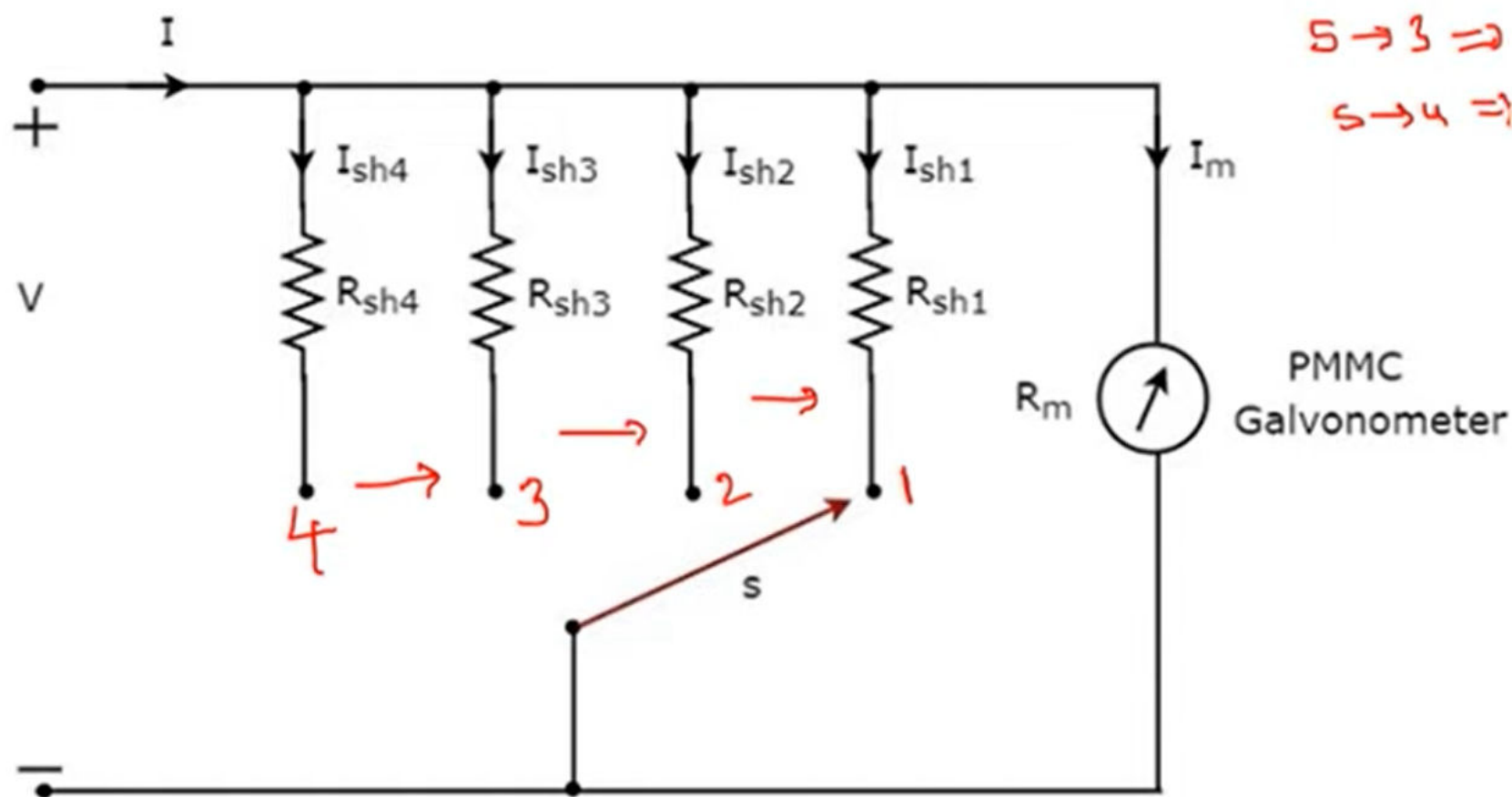

$$S \rightarrow 1 \Rightarrow R_{sh1}$$

$$S \rightarrow 2 \Rightarrow R_{sh2}$$

$$S \rightarrow 3 \Rightarrow R_{sh3}$$

$$S \rightarrow 4 \Rightarrow R_{sh4}$$

Problems

1. A 1mA meter movement with an internal resistance of 100Ω is to be converted into a 0-10 mA, 50mA and 100mA. Calculate the value of shunt resistance required.



Problems


1. A 1mA meter movement with an internal resistance of 100Ω is to be converted into a 0-10 mA, 50mA and 100mA. Calculate the value of shunt resistance required.

$$I_m = 1\text{mA}, R_m = 100\Omega, I_1 = 10\text{mA}, I_2 = 50\text{mA}, I_3 = 100\text{mA}.$$


$$R_{sh1} = \frac{I_m \cdot R_m}{I_1 - I_m} = \frac{1\text{m} \times 100}{10\text{m} - 1\text{m}} = \frac{0.1}{9\text{m}} = 11.1\Omega$$

$$R_{sh2} = \frac{I_m \cdot R_m}{I_2 - I_m} = \frac{1\text{m} \times 100}{50\text{m} - 1\text{m}} = \frac{0.1}{49\text{m}} = 2.04\Omega$$
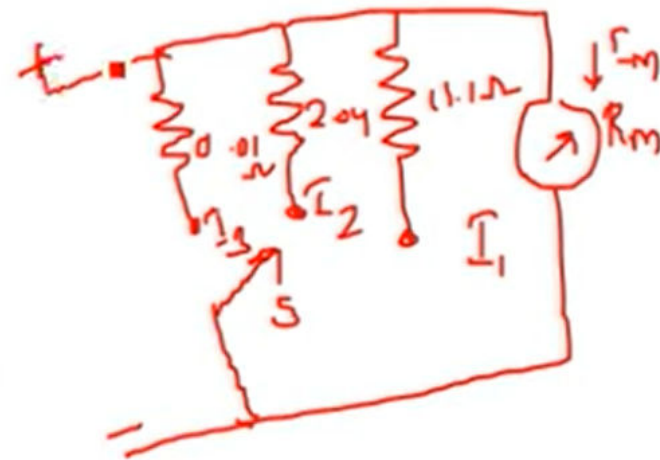
$$R_{sh3} = \frac{I_m \cdot R_m}{I_3 - I_m} = \frac{1\text{m} \times 100}{100\text{m} - 1\text{m}} = \frac{0.1}{99\text{m}} = 0.01\Omega$$



DC Voltmeter

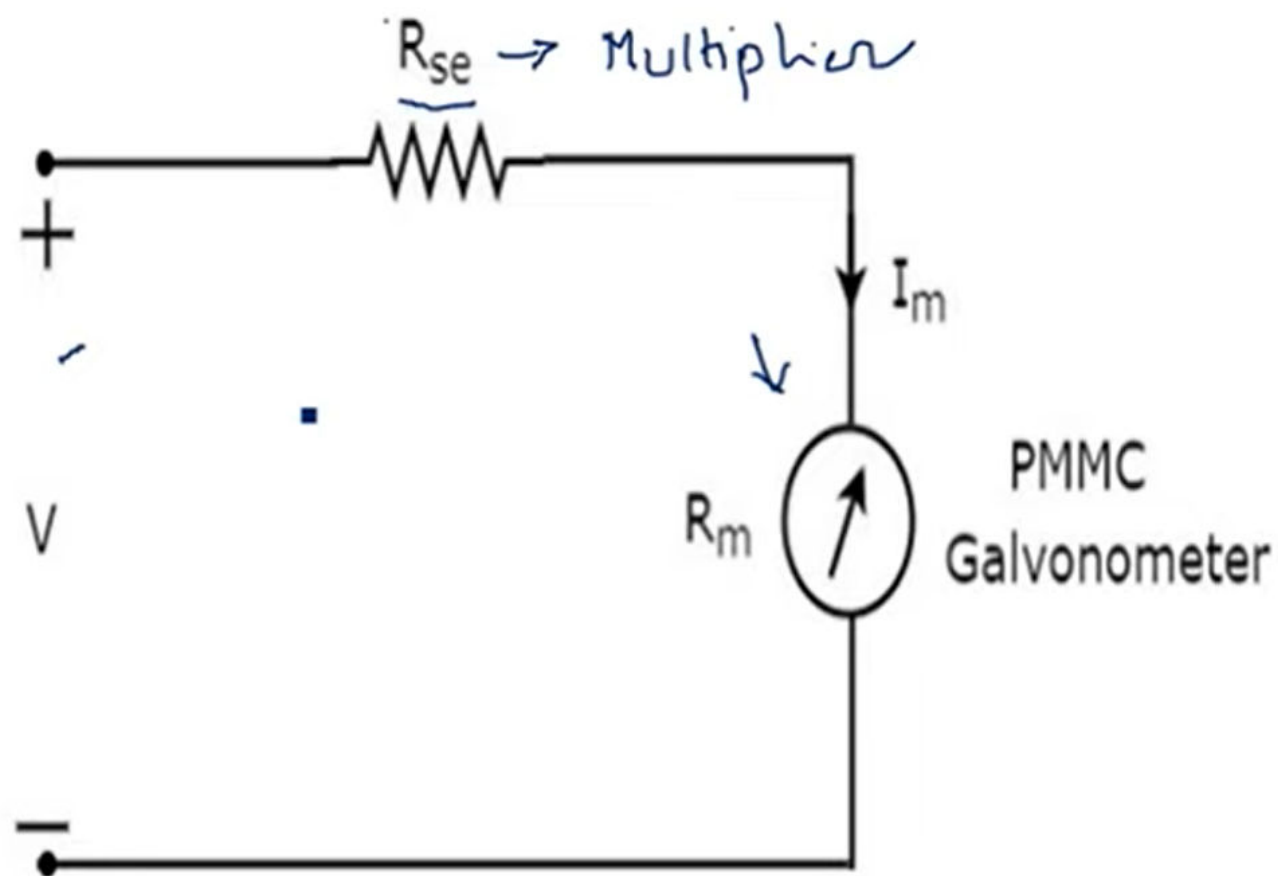

I_m = full scale deflection current of the movement (I_{fsd})

R_m = internal resistance of the movement

R_s = multiplier resistance

V = full range voltage of the instrument

Calculation of Multiplier resistance


$$R_{sh} \left(\frac{V}{I_m}, I_m, R_m \right)$$
$$R_{sh} = \frac{I_m \cdot R_m}{I - I_m}$$

$$V = I_m (R_s + R_m) \checkmark$$

$$R_s = \frac{V - I_m R_m}{I_m} = \frac{V}{I_m} - R_m$$

$$R_s = \frac{V}{I_m} - R_m \checkmark$$
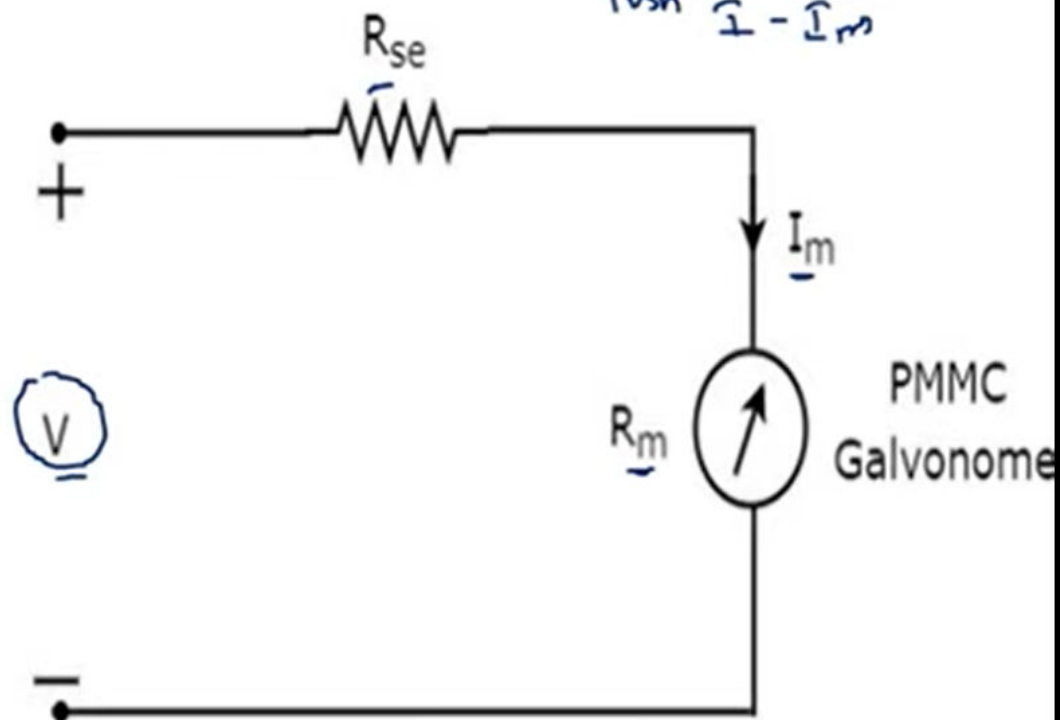
$$R_s \left(\frac{V}{I_m}, I_m, R_m \right)$$



Example problem

1. A basic D' Arsonval movement with a full-scale deflection of 50 μ A and internal resistance of 500 Ω is used as a DC voltmeter. Determine the value of the multiplier resistance needed to measure a voltage range of 0-10V.

Example problem

1. A basic D' Arsonval movement with a full-scale deflection of 50 μA and internal resistance of 500 Ω is used as a DC voltmeter. Determine the value of the multiplier resistance needed to measure a voltage range of 0-10V.

$$I_m = 50 \mu\text{A}, R_m = 500 \Omega, V = 10\text{V}, R_s = ?$$

$$\begin{aligned} R_s &= \frac{V}{I_m} - R_m = \frac{10}{50 \times 10^{-6}} - 500 \\ &= 0.2 \times 10^6 - 500 \\ R_s &= \underline{199.5 \text{ K}\Omega} \end{aligned}$$

$$\begin{aligned} R_{sh} &\rightarrow \Omega \\ R_s &\rightarrow \text{K}\Omega \\ &= \cdot = \end{aligned}$$

Sensitivity

$$S \propto \frac{1}{I_{fsd}} \quad S = \frac{1}{I_m}$$

- Sensitivity and voltmeter range can be used to calculate the multiplier resistance, R_s of a DC voltmeter.

$$R_s = (S \times \text{Range}) - R_m$$

$$R_s = \frac{V}{I_m} - R_m = \underset{\substack{\uparrow \\ \text{Range}}}{SV} - R_m$$

- From example:

$$I_m = 50 \mu A, R_m = 500 \Omega, \text{Range} = 10V$$

Sensitivity,

$$S = \frac{1}{I_m} = \frac{1}{50 \mu A} = 20 k\Omega/V$$

$$\begin{aligned} \text{So, } R_s &= (20 k\Omega/V \times 10V) - 500 \Omega \\ &= 199.5 k\Omega \end{aligned}$$