
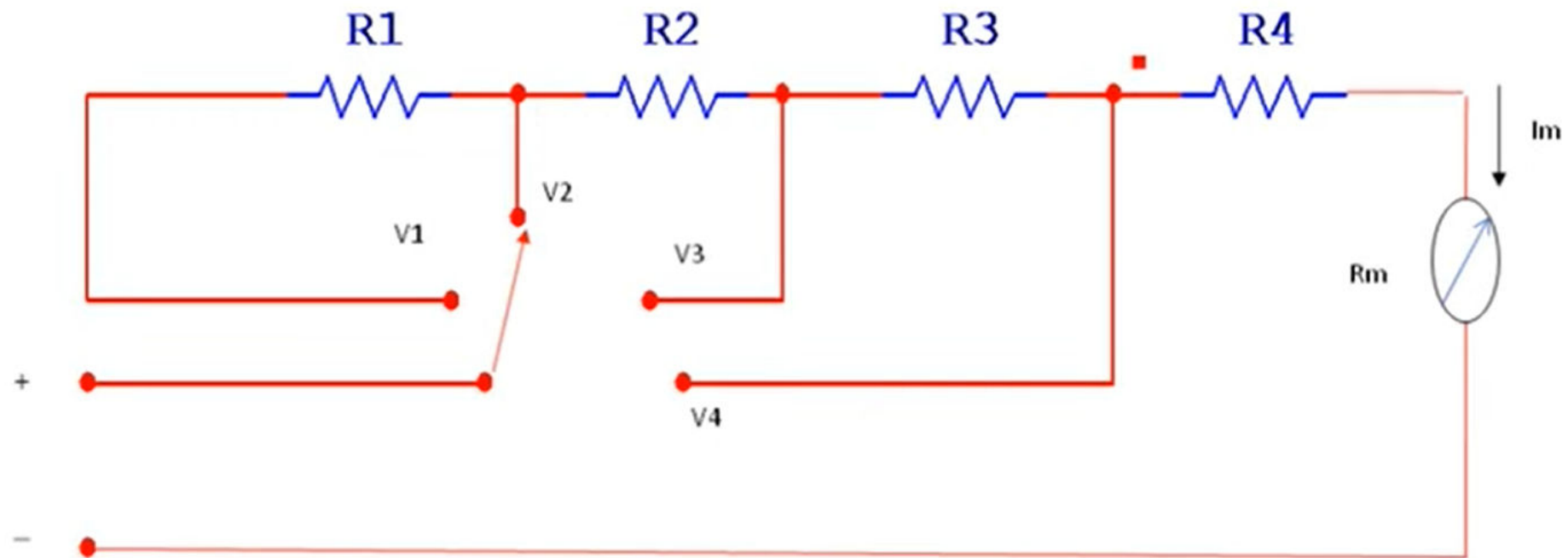


Multi-range DC voltmeter

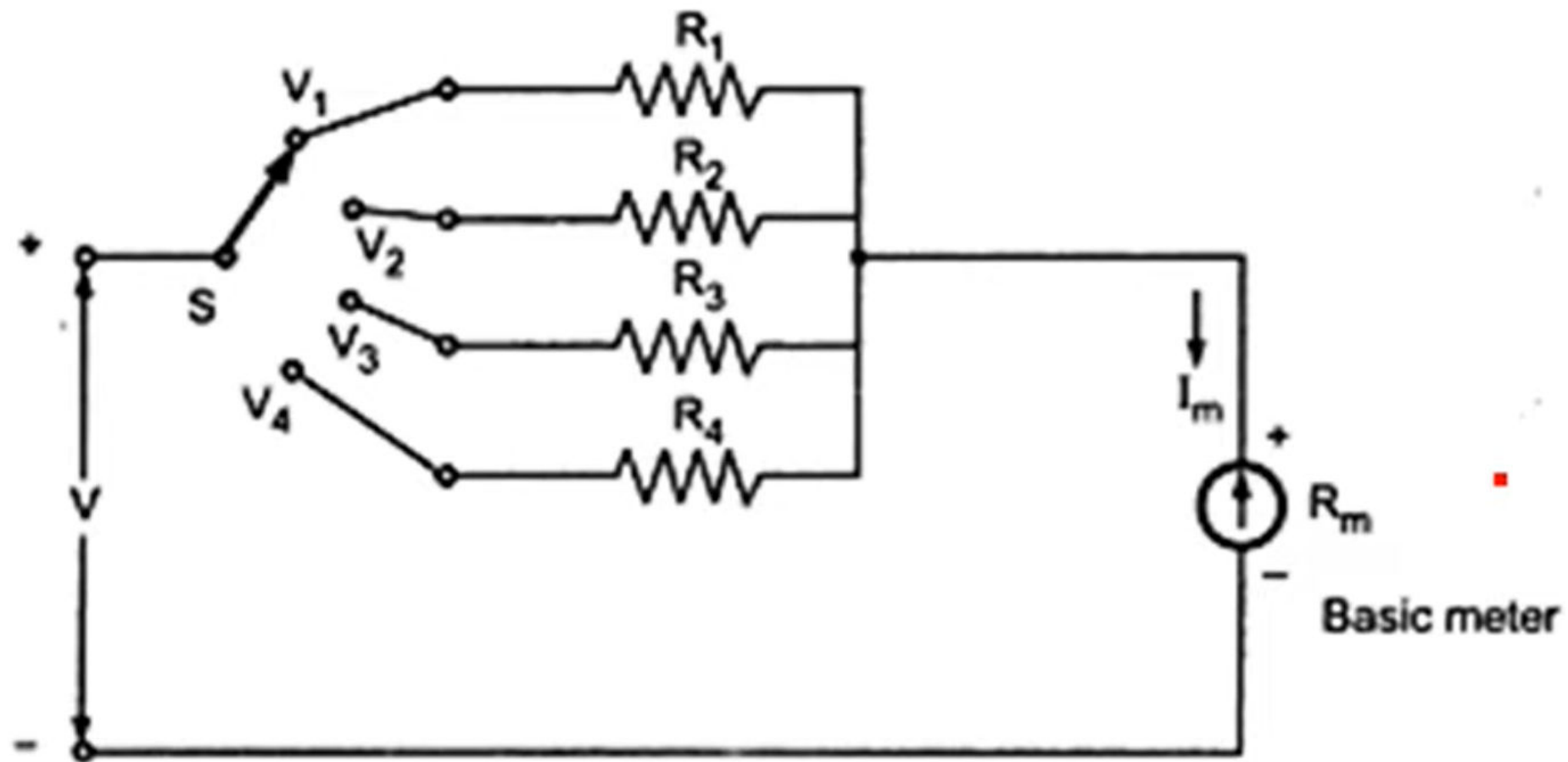- A DC voltmeter can be converted into a multirange voltmeter by connecting a number of resistors (multipliers) in series with the meter movement.
- A practical multi-range DC voltmeter is shown in Figure.



Other type of Multi-range DC voltmeter



Example problem

1. Convert a basic D' Arsonval movement with an internal resistance of 50Ω and a full scale deflection current of 2 mA into a multirange dc voltmeter with voltage ranges of 0-10V, 0-50V, 0-100V and 0-250V.

Example problem

1. Convert a basic D' Arsonval movement with an internal resistance of 50Ω and a full scale deflection current of 2 mA into a multirange dc voltmeter with voltage ranges of $0\text{-}10\text{V}$, $0\text{-}50\text{V}$, $0\text{-}100\text{V}$ and $0\text{-}250\text{V}$.

$$I_m = 2\text{ mA}, R_m = 50\Omega, V_1 = 10\text{V}, V_2 = 50\text{V}, \\ V_3 = 100\text{V}, V_4 = 250\text{V}.$$


Shunt:-


$$\text{Case 1: } S \rightarrow V_1 \quad R_{S1} = \frac{V_1}{I_m} - R_m = \frac{10}{2\text{ mA}} - 50 \\ = 4.95\text{ k}\Omega.$$

$$\text{Case 2: } S \rightarrow V_2, \quad R_{S2} = \frac{V_2}{I_m} - R_m = 24.95\text{ k}\Omega$$

$$\text{Case 3: } S \rightarrow V_3 \quad R_{S3} = \frac{V_3}{I_m} - R_m = 49.95\text{ k}\Omega$$
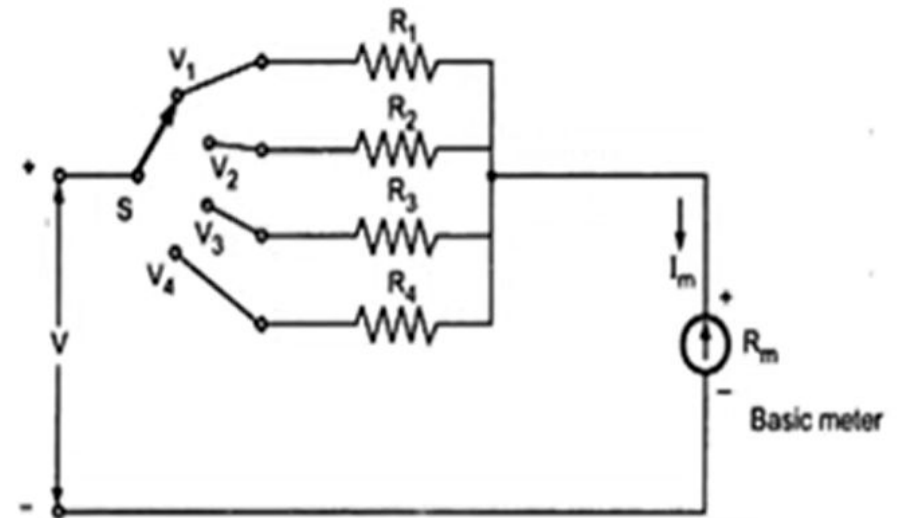
$$\text{Case 4: } S \rightarrow V_4; \quad R_{S4} = \frac{V_4}{I_m} - R_m = 124.95\text{ k}\Omega$$



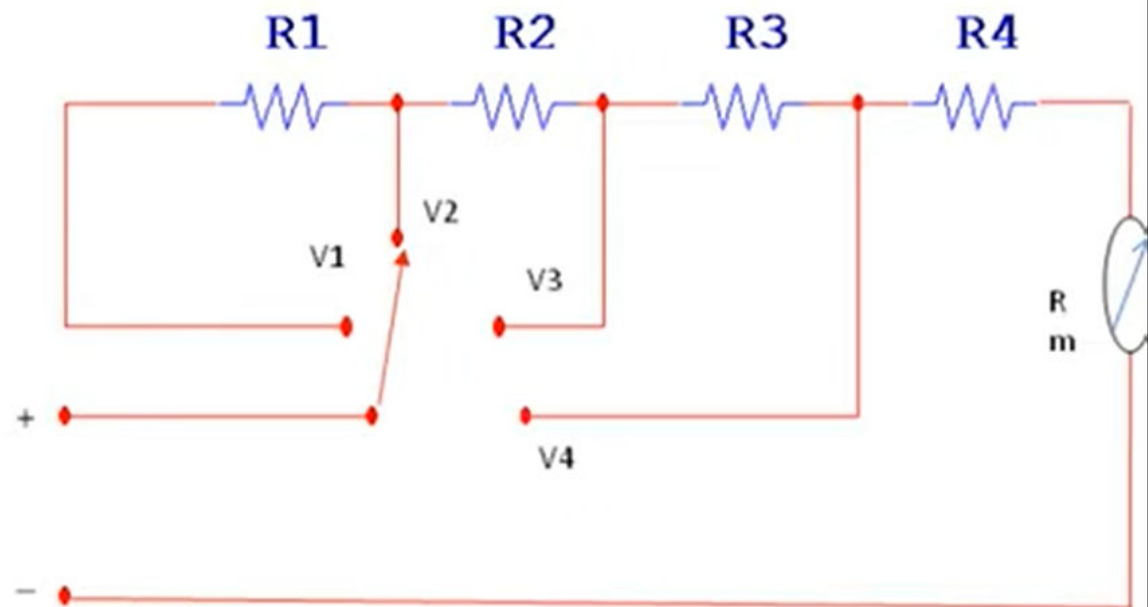

Series

Case 1: $S \rightarrow V_4$; $R_4 = \frac{V_4}{I_m} - R_m$
 $= 4.95 \text{ k}\Omega$

Case 2: $S \rightarrow V_3$; $R_3 = ?$

Total Voltage $\rightarrow V_3$

" Current $\rightarrow I_m$

" Resistance $\rightarrow R_T$

$$R_T = R_3 + R_4 + R_m.$$


$$R_T = \frac{V_3}{I_m} = ?$$

$$R_3 = 20 \text{ k}\Omega$$

Case 3: $S \rightarrow V_2$, $R_2 = ?$

$$R_T = R_2 + R_3 + R_4 + R_m$$

$$R_T = \frac{V_2}{I_m}$$

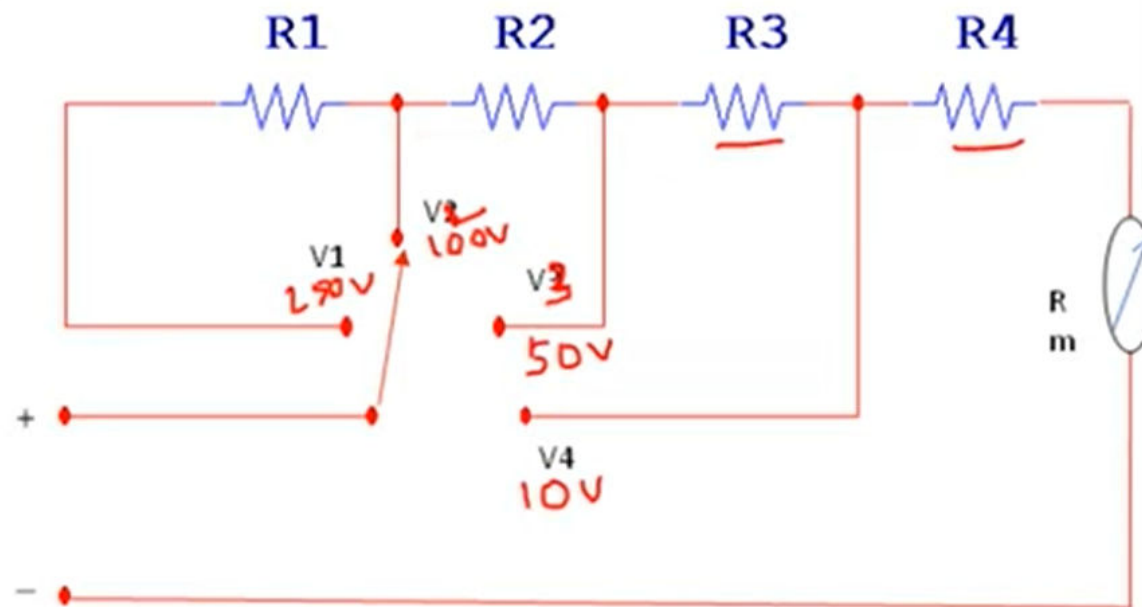

$$R_2 = 25 \text{ k}\Omega$$

Case 4: $S \rightarrow V_1$; $R_1 = ?$

$$R_T = R_1 + R_2 + R_3 + R_4 + R_m$$

$$R_T = \frac{V_1}{I_m}$$

$$R_1 = 75 \text{ k}\Omega$$

Shunt

$$\rightarrow R_1 = 4.95 \text{ k}\Omega \text{ (one)}$$

$$\rightarrow R_2 = \underline{24.95 \text{ k}\Omega} \text{ (one)}$$

$$\rightarrow R_3 = \underline{49.95 \text{ k}\Omega}$$

$$\rightarrow R_4 = 124.95 \text{ k}\Omega$$

Series

$$\{ R_1 = \underline{4.95 \text{ k}\Omega} \text{ (one)}$$

$$R_2 = \underline{20 \text{ k}\Omega} \text{ (two)}$$

$$R_3 = \underline{25 \text{ k}\Omega}$$

$$R_4 = \underline{75 \text{ k}\Omega}$$